

NAME: PRERNA SUNIL JADHAV  
 SAP ID: 60004220127  
 BRANCH: COMPUTER ENGINEERING

COURSE CODE: DJ19CEC805

COURSE: DIGITAL ELECTRONICS

### ASSIGNMENT

Q1 Convert and present  $(45)_{10}$  in Hexadecimal, Binary and Octal system.

Soln:

To convert  $(45)_{10}$  to Binary divide 45 by 2 as Binary has base 2 until quotient is 0.

Quotient = Remainder

$$\begin{array}{r}
 45 \\
 \underline{\div 2} \\
 22 \quad R \quad 1 \\
 \underline{\div 2} \\
 11 \quad R \quad 0 \\
 \underline{\div 2} \\
 5 \quad R \quad 1 \\
 \underline{\div 2} \\
 2 \quad R \quad 1 \\
 \underline{\div 2} \\
 1 \quad R \quad 0 \\
 \underline{\div 2} \\
 0 \quad R \quad 1
 \end{array}$$

$$\therefore (45)_{10} = (101101)_2$$

To convert into octal,

$$(45)_{10} = \underline{\underline{101101}}_2 = 0(55)_8$$

↓ ↓  
5 5

To convert into hexadecimal,

$$(45)_{10} = \underline{\underline{101101}}_2 = (2D)_{16}$$

2 D

Q2

a) Perform the following operation using 2's complement

$$(76)_8 - (22)_{16}$$

Soln:

(Converting  $(76)_8$  and  $(22)_{16}$  into Decimal)

$$(76)_8 = 7 \times 8^1 + 6 \times 8^0$$

$$= 56 + 6 = (62)_{10}$$

$$(22)_{16} = 2 \times 16^1 + 2 \times 16^0$$

$$= 32 + 2 = (34)_{10}$$

(converting Decimal to Binary)

Quotient	Remainder	Quotient	Remainder
$\frac{62}{2}$	31	0	↑
$\frac{31}{2}$	15	1	↑
$\frac{15}{2}$	7	1	↑
$\frac{7}{2}$	3	1	↑
$\frac{3}{2}$	1	1	↑
$\frac{1}{2}$	0	1	↑

$\frac{34}{2}$	17	0	↑
$\frac{17}{2}$	8	1	↑
$\frac{8}{2}$	4	0	↑
$\frac{4}{2}$	2	0	↑
$\frac{2}{2}$	1	0	↑
$\frac{1}{2}$	0	1	↑

$$\therefore (62)_{10} = (111110)_2$$

$$\therefore (34)_{10} = (100010)_2$$

Now,

Performing 2's complement of  $(100010)_2$

$$1\text{'s complement} \rightarrow 011101 + 8A = Y$$

$$2\text{'s complement} \rightarrow 011110 + 8A = Y$$

Now, performing subtraction using 2's complement

$$\therefore (76)_8 \rightarrow (62)_{10} \rightarrow 111110$$

$$\therefore (22)_{16} \rightarrow (34)_{10} \rightarrow 2\text{'s comp} \rightarrow (+)111110$$

carry  $\rightarrow \boxed{1}$  011100

Here, carry generated is 1, which indicates that the answer is positive and need to ignore it.

$$\therefore (11100)_2 = (28)_{10}$$

$$\therefore (76)_8 - (22)_{16} = (28)_{10} = (11100)_2$$

Q3

- a) Use boolean laws to minimize and then implement using basic gates.

$$Y = AB + BC + ABC + ABB$$

Soln:

$$Y = AB + BC + ABC + ABB$$

$$Y = AB + BC + ABC + \underline{AB} \quad \dots [\because A \cdot A = A]$$


$$Y = AB + BC + ABC \quad \dots [\because A + A = A]$$

$$Y = AB + BC (1 + A)$$

$$Y = AB + BC \quad \dots [1 + A = 1]$$

$$Y = B(C + A)$$

Implementation using basic gates.

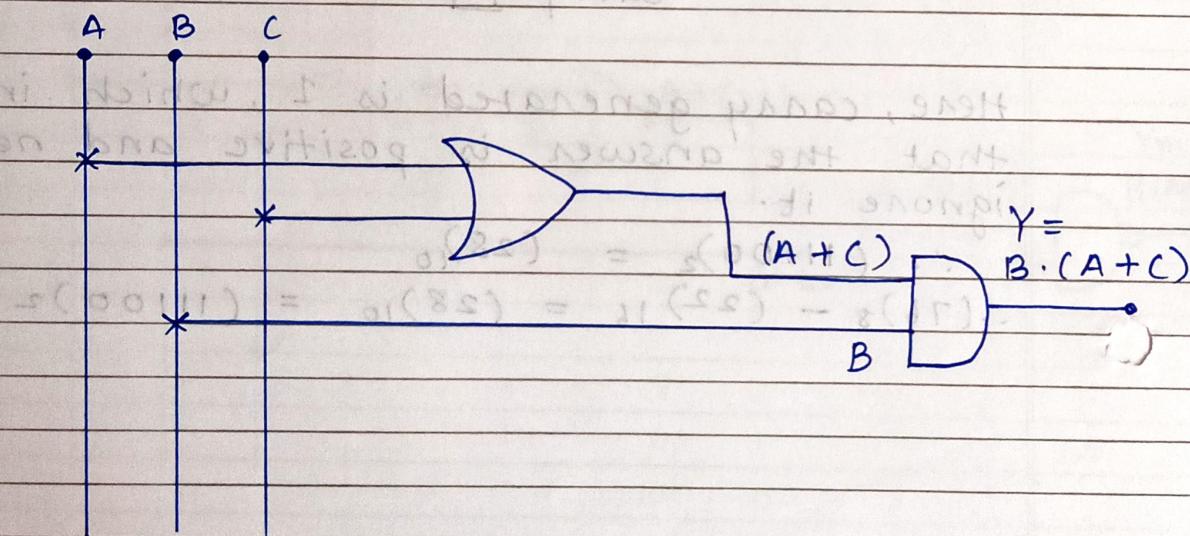

Q4  
B)

1. Minimize and implement following SOP using universal gates

$$Y = AB + BC + ABC + ABB$$

Soln:  $Y = AB + BC + ABC + \underline{ABB}$

$$Y = AB + BC + ABC + AB \dots [\because A \cdot A = A]$$


$$Y = AB + BC + ABC \dots [\because A + A = A]$$

$$Y = AB + BC(1 + A)$$

$$Y = AB + BC$$

$$Y = B(A + C)$$

Implementation using universal gates.

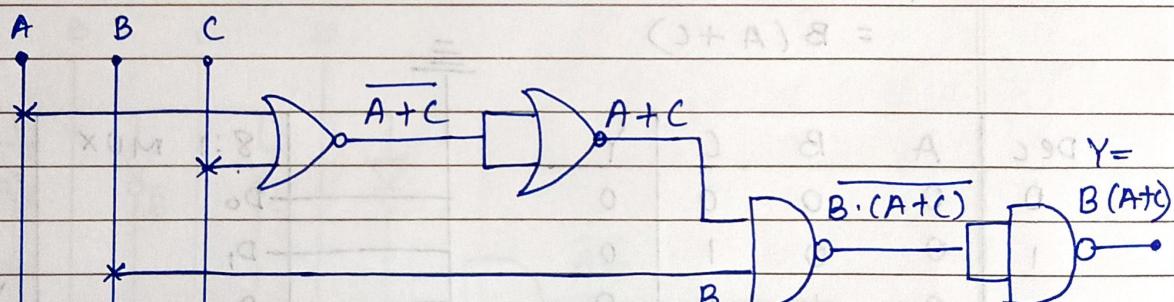

Q4)

a)

2. Minimize and implement following SOP using Multiplexer

$$Y = AB + BC + ABC + ABB$$

Soln

$$Y = AB + BC + ABC + ABB$$

$$Y = AB + BC + ABC + AB \quad [\because A \cdot A = A]$$

$$Y = AB + BC + ABC \quad [\because A + A = A]$$

$$Y = AB + BC (1+A)$$

$$Y = AB + BC \quad [\because 1+A=1]$$


$$Y = B(A+C)$$

Implementation using multiplexer

$$Y = AB + BC + ABC + ABB$$

$$= B(A+C)$$

Dec	A	B	C	Y
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

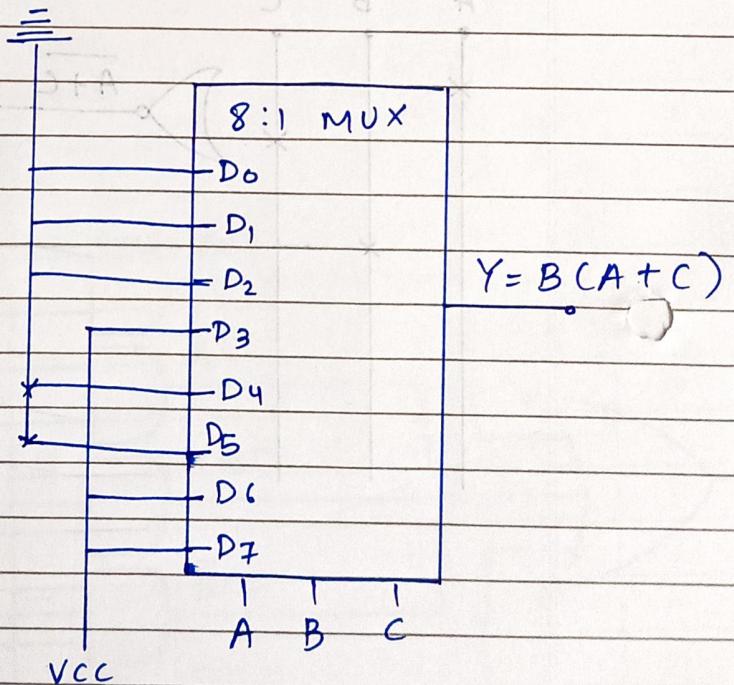

Q5

a)

i) Simplify using K Map and Implement using basic gates.


$$Y = \sum m(0, 1, 2, 3, 4, 5, 8, 11, 13, 15)$$

Soln:

AB \ CD	00	01	11	10	
00	1	1	1	1	I
01	1	1	1	0	II
11	1	1	1	1	III
10	1	0	1	1	IV

$\Rightarrow Y = \bar{B}\bar{C}\bar{D}$
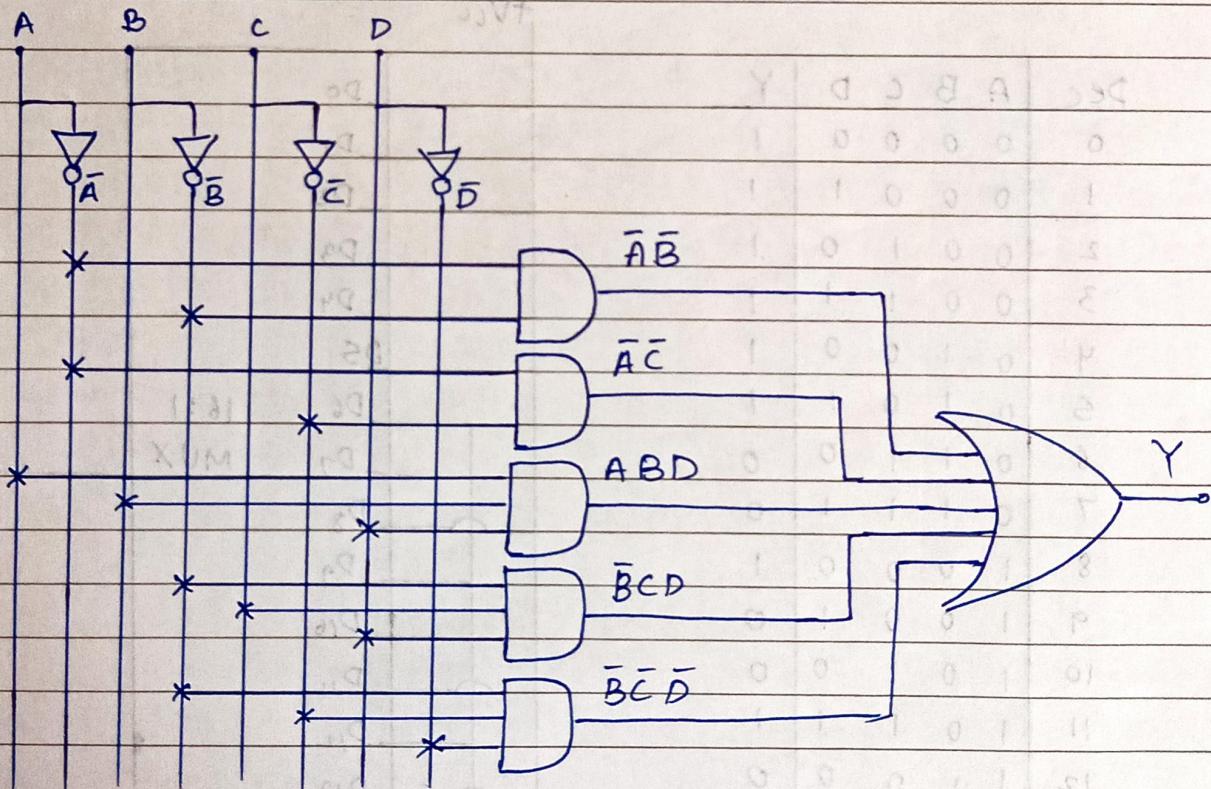
$$\therefore Y = \bar{A}\bar{B} + \bar{A}\bar{C} + ABD + \bar{B}CD + \bar{B}\bar{C}\bar{D}$$



Q5

a)

2. Simplify using K-map and implement using multiplexer (use either single 16:1 or use 2 units of 8:1)

$$Y = \sum m(0, 1, 2, 3, 4, 5, 8, 11, 13, 15)$$

Soln:

AB	CD	00	01	11	10		
00	00	1	1	1	1	I	$\bar{A}\bar{B}$
01	01	1	1	1	0	II	$\bar{A}C$
11	11	1	1	1	1	III	$ABD$
10	10	1	0	1	1	IV	$\bar{B}CD$
						V	$\bar{B}\bar{C}\bar{D}$

$$\therefore Y = \bar{A}\bar{B} + \bar{A}C + ABD + \bar{B}CD + \bar{B}\bar{C}\bar{D}$$

+Vcc

